

The 3rd IEEE International Conference on DC Microgrids

May 20-23, 2019

Matsue, Japan

An Efficiency-Focused Design of Direct-DC Loads in Buildings

Daniel Gerber, Richard Liou, Richard Brown
dgerb@berkeley.edu
Berkeley, CA, USA

DC Microgrids in Buildings




Motivation

- DC buildings are efficient
 - Up to 14% more efficient than AC
 - Most loads are internally DC
- Barriers to entry
 - Lack of DC loads on the market
 - Many 380 V DC demonstrations use loads that are not designed for 380 V
- This work explores how DC loads can be designed to leverage the benefits of DC distribution


Categories of Loads

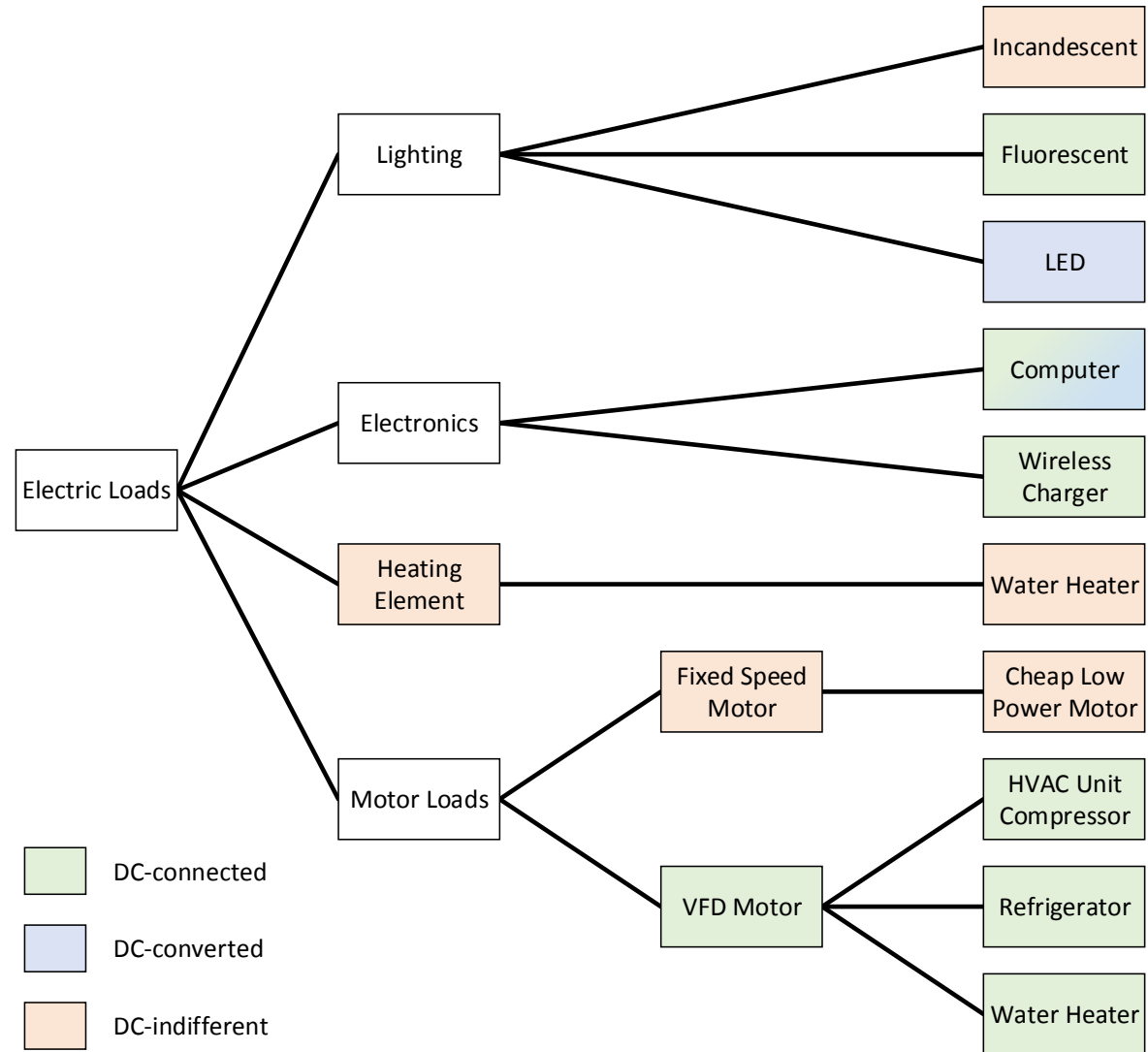- **DC-connected:**
Internal DC stage of these loads can be connected or hardwired directly to the DC distribution
- **DC-converted:**
Requires a DC/DC converter in order to connect to the DC
- **DC-indifferent:**
Equivalent benefits with AC or DC input




Motor Loads – BLDC Motors

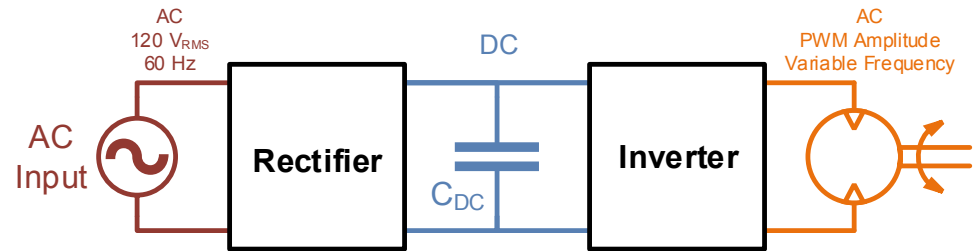- The most efficient motor loads use variable speed drive brushless DC (BLDC) motors
- AC BLDC motors have a rectifier, internal DC capacitors, and inverter
- The internal DC caps can connect directly to DC distribution, avoiding the rectification stage







AC BLDC Motor Load

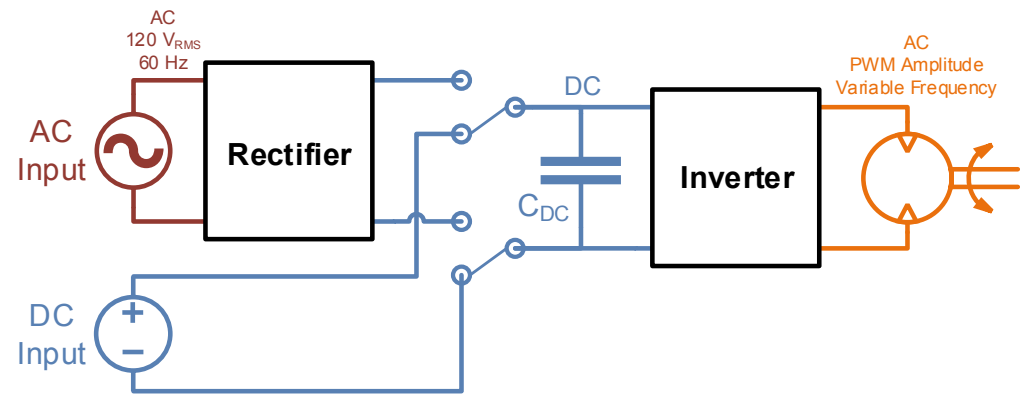

Internal DC Caps can connect to DC distribution


Motor Loads – Bath Fan

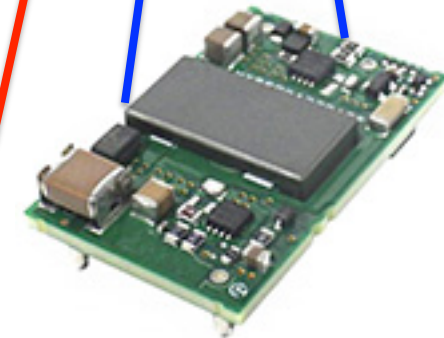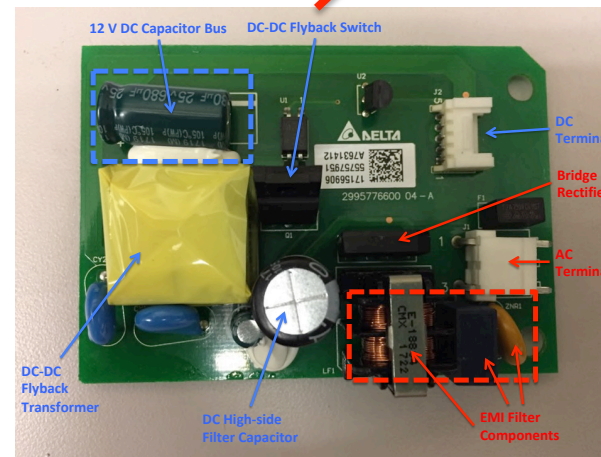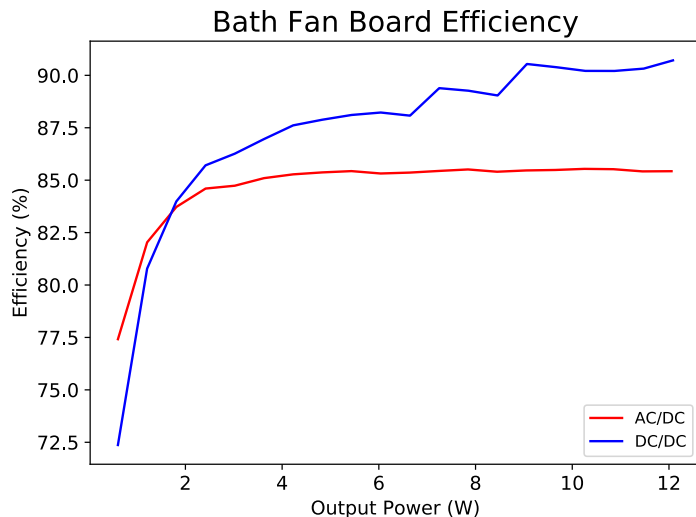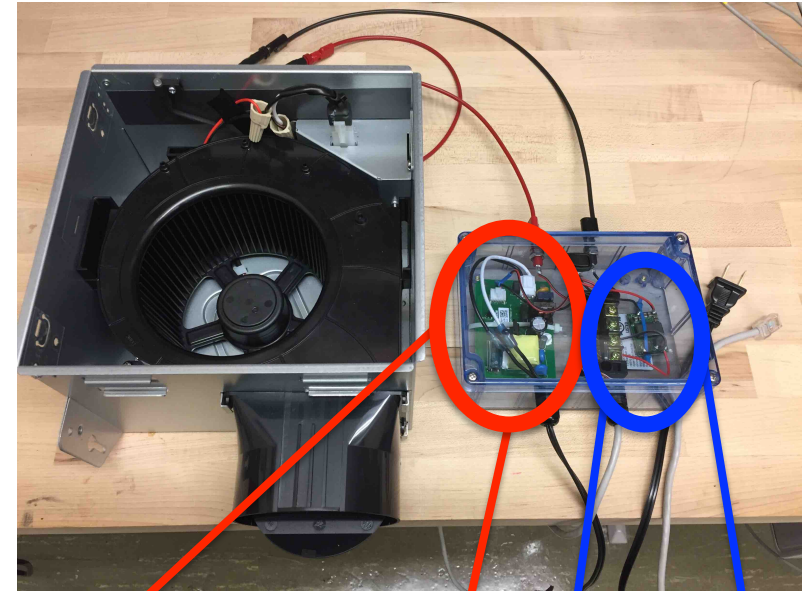- Internal DC bus: 12 V
 - Modify for 48 V PoE input
1. Use a 48/12 V DC/DC converter:
-4% consumption
 2. Redesign inverter/motor for 48 V:
potentially -14% consumption




Motor Loads – DC Bus Voltage

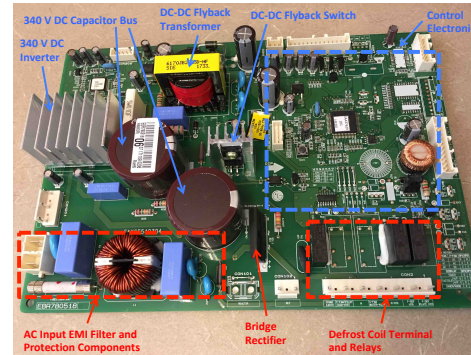
- No need for DC/DC converter if DC bus voltage equals DC distribution voltage
- BLDC motors can be redesigned for any DC bus voltage
 - Replace inverter if needed
 - High-voltage motors will use thinner wire and more turns on the stator coil
 - Winding area and loss is equivalent




340 V Inverter Board

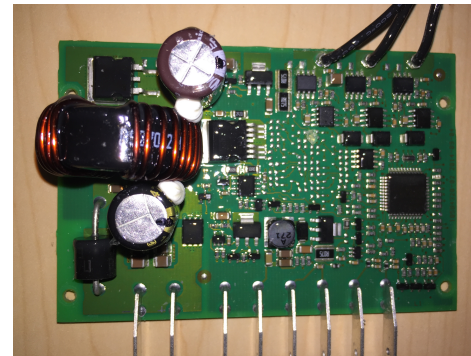

24 V Inverter Board

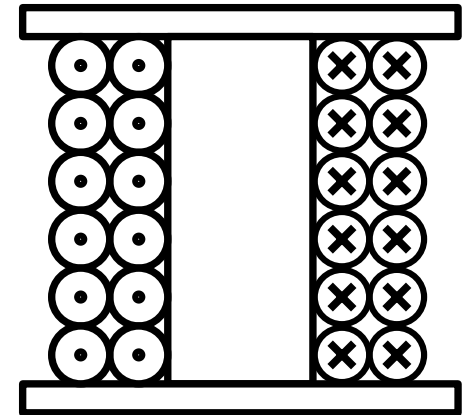


High-voltage DC bus

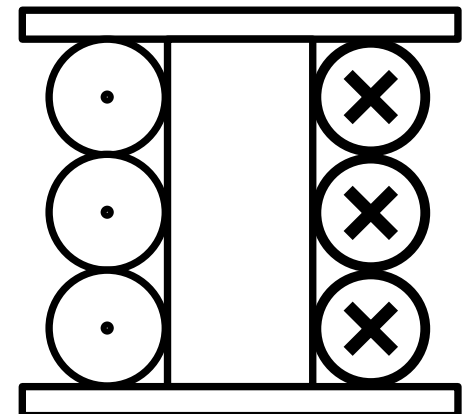

Low-voltage DC bus


Lighting – Today’s Integration Paradigm

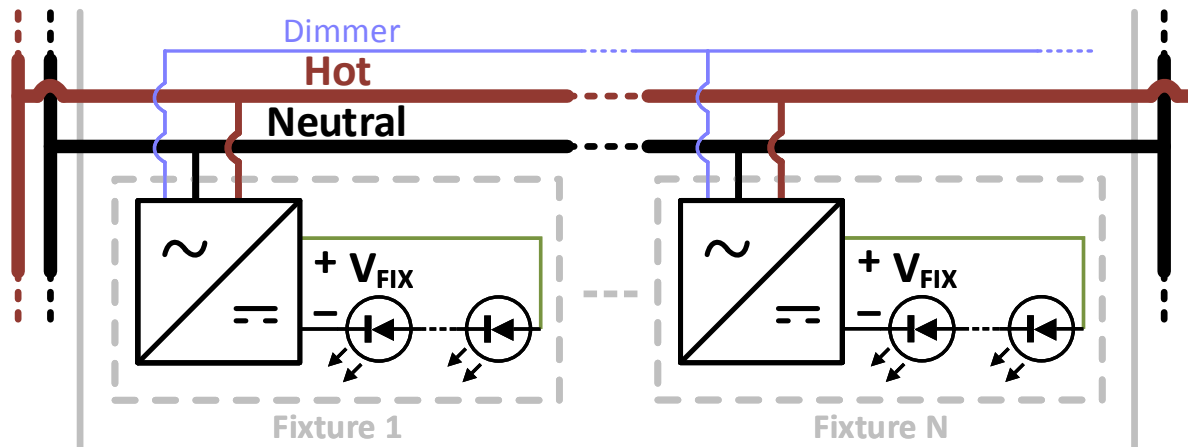- Most LED drivers are integrated into bulb, allows plug-and-play
 - Pros:
 - Plug-and-play compatibility
 - Cons:
 - High conversion ratio is inefficient
 - Components must tolerate high voltage: bulky and expensive
- The problems of integration are even worse at 380 V DC
- We propose (1) remote drivers, (2) series fixtures





Lighting – Why Remote Drivers?

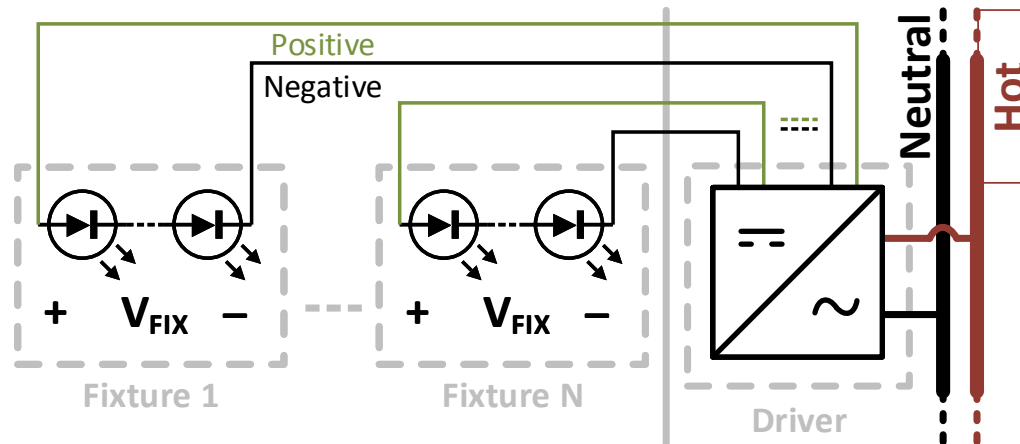- Reduces life-cycle cost by up to 58%
 - Separating the driver from the fixture doubles the fixture's life span (40%)
 - Clever driver placement reduces maintenance costs for replacing light bulbs, especially in high bay (30%)
- Easy to add ancillary services
 - Wireless dimming
 - Battery backup
- Most remote drivers on the market wire fixtures in parallel



Lighting – Why Series Fixtures?

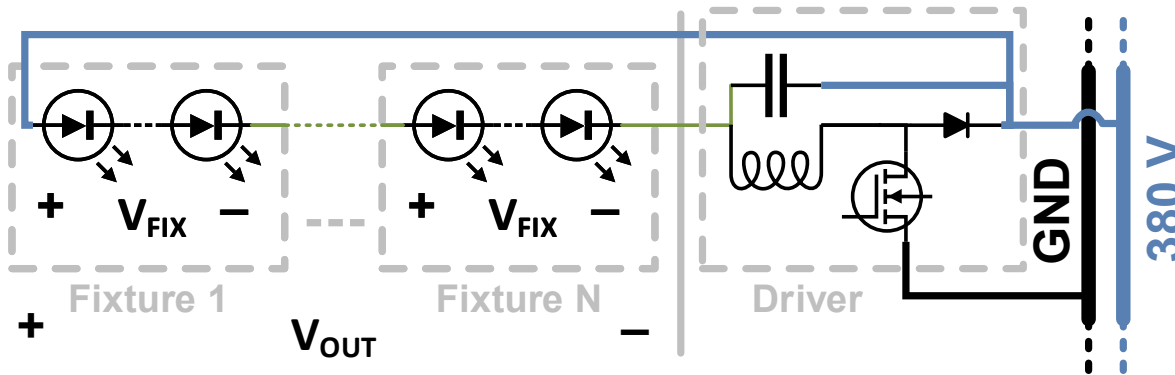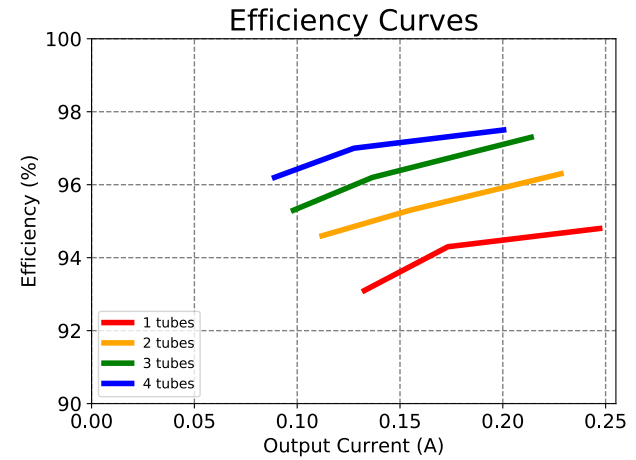- Reduces life-cycle cost (10%-20%)
 - One driver powers many fixtures
- Improves efficiency (>98%)
 - Can stack fixtures such that $N \cdot V_{FIX}$ is close to 380 V
 - In prototype, adding extra bulbs increased efficiency from 94% to 98%



Conclusion

- Design DC loads to avoid unnecessary conversion stages
- Motor loads can be easily redesigned with any DC bus voltage
- Zone lighting at 380 V can benefit from series remote drivers

Thank you!



An Efficiency-Focused Design of Direct-DC Loads in Buildings
Daniel Gerber, Richard Liou, Richard Brown




6/29/2017
Page 11

Project Goals


- Categorize loads based on how they benefit from DC
- Modify several AC loads for DC input and demonstrate reduced consumption
- Determine how to optimally design various classes of loads for DC input

Motor Loads - Sizing the DC Capacitors

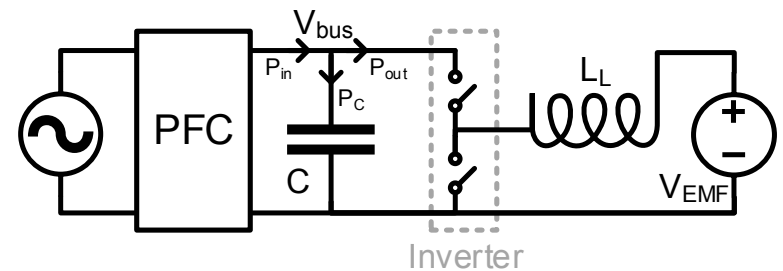- Reasons for DC capacitors
 - Filter PWM ripple (20-100 kHz)
 - Provide a buffer for transients in load current
 - Filter 120 Hz AC ripple from the DC bus
- DC loads do not need to filter 120 Hz AC ripple
- DC loads allow for smaller DC capacitors for both motor loads and lighting



Model to analyze AC and PWM ripple

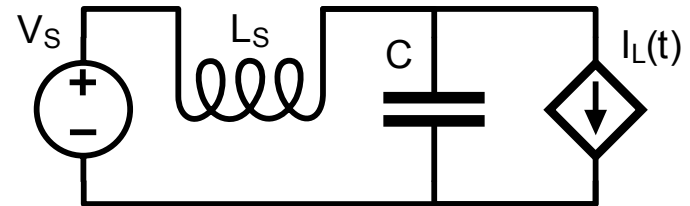


Model to analyze load transients


C (uF)	AC Ripple (V)	PWM Ripple (V)	Transient Ripple (V)
10.0	78.02	3.32	0.82
100.0	7.8	0.33	0.26
1000.0	0.78	0.03	0.08

Lighting – Low Voltage

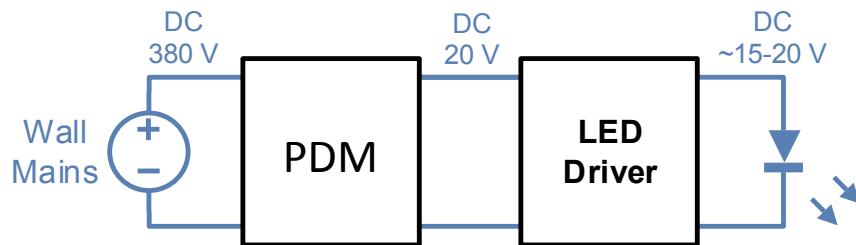- Many task lamps or PoE fixtures have their own integrated LED drivers
 - Two conversion stages: power distribution module (PDM) and LED driver
- Allowing the PDM to act as an LED driver reduces conversion stages
- USB task lamp
 - USB charging station acts as LED driver
 - Uses Qualcomm quick charge to control current



Fixture with integrated LED driver

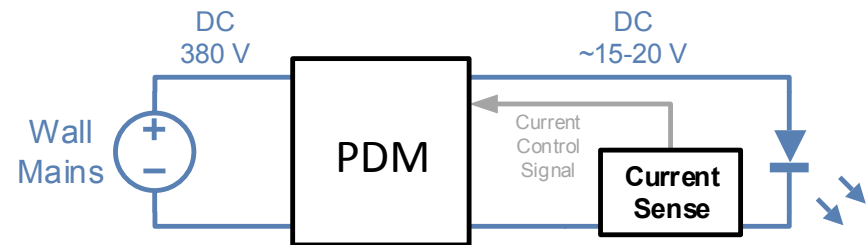

PDM acts as LED driver

Bypass Circuit

